

Design Idea DI-76

LinkSwitch®

3.1 W Low Parts Count Power Supply



Application	Device	Power Output	Input Voltage	Output Voltage	Topology
Appliance/Industrial Control	LNK520P	3.1 W	100-375 VDC	12 V	Flyback

Design Highlights

- Replaces a linear transformer based power supply at the same or lower cost, but with much better performance
- High Efficiency: >75% at >100 mA of load current
- Primary side regulated: requires no optocoupler
- <300 mW no-load power consumption at 375 VDC
- Very low parts count: only 9 components!
- 12 V output: ideal for driving motors, relays, or SCRs

Operation

The very low parts count *LinkSwitch* flyback circuit shown below can be used as a general-purpose power supply or linear adapter replacement.

The design provides regulated output voltage during normal loads as well as a soft output-current limit during overload conditions (such as a stalled motor or defective relay). Adding to this, the other *LinkSwitch* self-protection features of auto-

restart (for hard short circuits) and thermal shutdown effectively produce a very rugged design.

LinkSwitch derives all feedback information from the primary side, thus no optocoupler is required. During output diode (D4) conduction, the output voltage is reflected through the transformer turns ratio, providing a primary feedback voltage (V_{OR}), which is rectified by diode D3 and held by capacitor C4. Resistor R3 limits the effects of transformer leakage on the feedback voltage. Resistor R2 feeds the V_{OR} signal as a current to the CONTROL pin of the *LinkSwitch*, controlling duty cycle (and primary current limit during overload conditions). When there is little or no feedback signal (such as a short circuit) the *LinkSwitch* goes into auto-restart, limiting output current to approximately 40 mA.

Capacitor C3 provides device decoupling. The extra winding on pin 3 of T1 is a shield that reduces EMI.

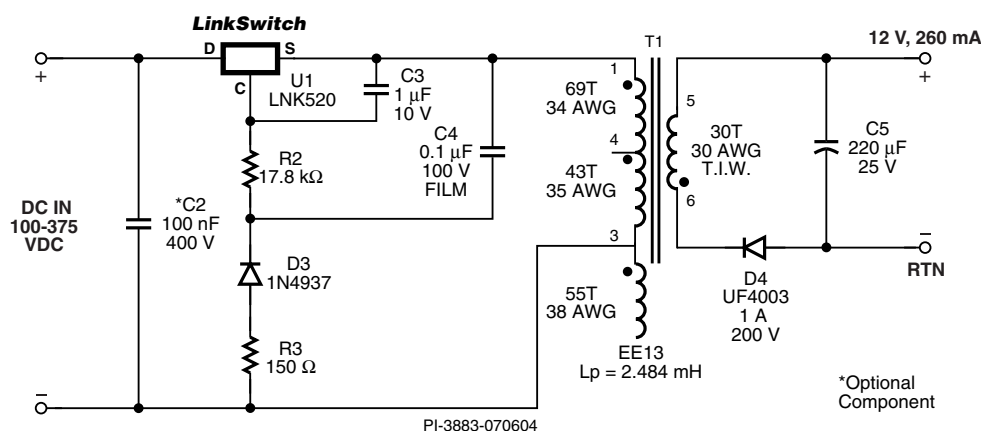


Figure 1. DC-Input, Isolated LinkSwitch 3.12 W Flyback Converter.

Key Design Points

- The value of C3 (1 μ F) allows time for the output voltage to develop at startup.
- A larger R3 value will provide flatter voltage regulation if a higher no-load voltage can be tolerated.
- A lower R2 value will reduce the output voltage while proportionally increasing the maximum output current.

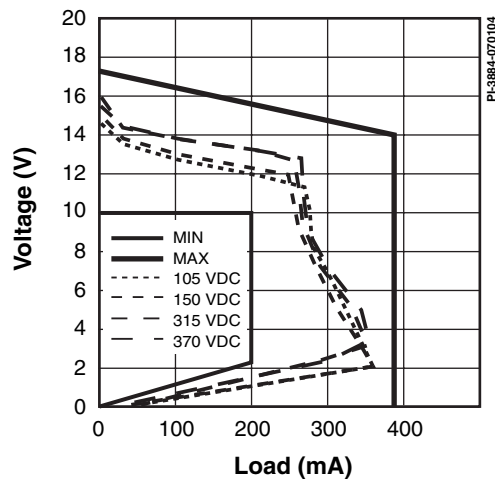


Figure 2. Output Regulation vs. Load Current Curves.

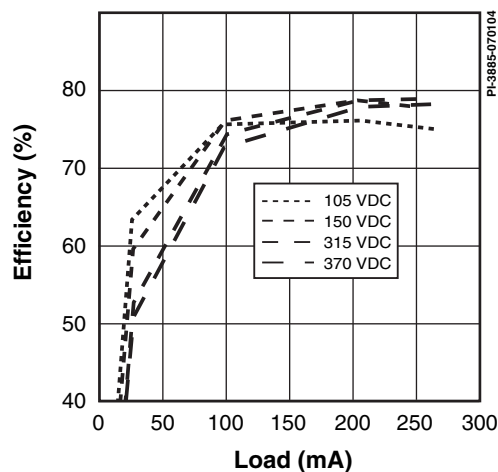


Figure 3. Efficiency vs. Output Current Curves.

- Output diode D4 needs a sufficient peak inverse voltage (PIV) rating for high line withstand, requiring an ultra-fast 200 V type (UF4003). For lower output voltages (PIV <100 V), Schottky diodes work well and enable improved efficiency.
- The *LinkSwitch* PIXIs spreadsheet tool included in *PI Expert*™ Design Software can be used to redesign the transformer for different output voltages.

TRANSFORMER PARAMETERS	
Core Material	TDK PC40 EE13, $A_{LG} = 199 \text{ nH/T}^2$
Bobbin	EE13 Horizontal 8-pin
Winding Details	Shield 1: 55 T, #38 AWG, 1 Layer Primary-1: 69 T, #34 AWG, 2 Layers Primary-2: 43 T, #35 AWG, 1 Layer Secondary: 30 T, #30 T.I.W., 2 Layers
Winding Order (pin numbers)	Shield 1: (3-Float), Primary-1 (1-4), Primary-2 (4-3), Secondary (6-5)
Primary Inductance	2484 μ H $\pm 10\%$
Primary Resonant Frequency	500 kHz (minimum)
Leakage Inductance	70 μ H (maximum)

Table 1. Transformer Design Parameters.

For the latest updates, visit www.powerint.com

Power Integrations may make changes to its products at any time. Power Integrations has no liability arising from your use of any information, device or circuit described herein nor does it convey any license under its patent rights or the rights of others. POWER INTEGRATIONS MAKES NO WARRANTIES HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATIONS, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS. The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

The PI logo, **TOPSwitch**, **TinySwitch**, **LinkSwitch** and **EcoSmart** are registered trademarks of Power Integrations. **PI Expert** and **DPA-Switch** are trademarks of Power Integrations. ©Copyright 2004, Power Integrations

Power Integrations

5245 Hellyer Avenue

San Jose, California 95138

MAIN PHONE NUMBER
+1 408-414-9200

APPLICATIONS HOTLINE
+1 408-414-9660

APPLICATIONS FAX
+1 408-414-9760

For a complete listing of worldwide sales offices,
please visit www.powerint.com

